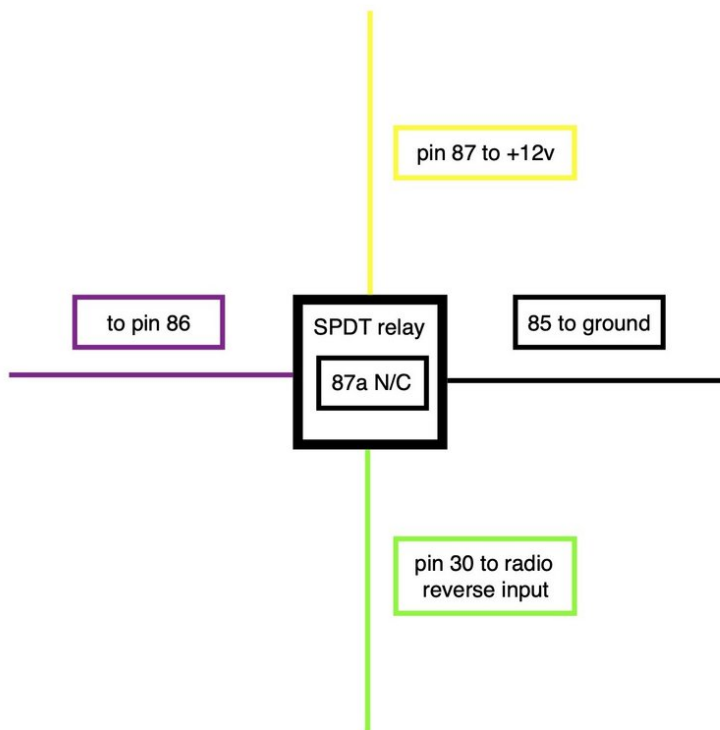



# 907 Camera Relay

Diagram for adding a relay to the 907 camera harness when the radio doesn't read the reverse trigger reliably.

Written By: Eric Masek



## Step 1 — 907 Camera Relay

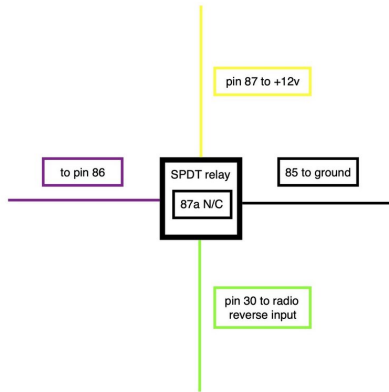

- Any 12v SPDT relay can be installed at the end of the purple lead in the 907CAM harness. The output from the relay will go to the radio reverse trigger as shown